

**REPORT BY:** Y.Sai Spandana Priya

**Project:** 0–5 mA Programmable Current Source (1 kΩ–10 kΩ load sweep)

**Tool:** LTspice 24.1.10


**Date:** 02/11/2025

## 1.Topology selection & justification

**Chosen topology:** Low-side NMOS pass element controlled by an op-amp with a series sense resistor ( $R_{sense}$ ) in the MOSFET source. The op-amp compares the user reference voltage ( $V_{in}$ ) to the sense node and drives the NMOS gate to force  $V_{sense} = V_{in}$ . The load ( $R_{load}$ ) is connected from the +60 V supply to the MOSFET drain.

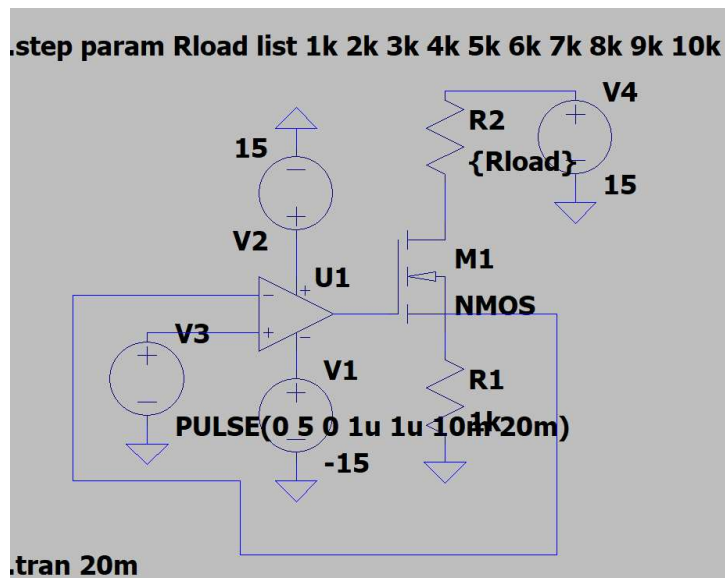**Why this topology?**

- **Simple, robust closed-loop** regulation: op-amp feedback enforces  $I_{out} = V_{in} / R_{sense}$  independent of  $R_{load}$  (as long as compliance is not violated).
- **Low-side NMOS** avoids gate bootstrap complications of a high-side N-MOS and allows the op-amp to drive the gate from a  $\pm$  supply easily.
- **Scalable:** MOSFET handles the power dissipation; a suitable part can support the 60 V supply and required currents.



## 2. Key Design Parameters and Component Choices

Parameter	Symbol	Value	Reason
<b>MOSFET</b>	Generic NMOS		For 1–10 k $\Omega$ compliance
<b>Sense Resistor</b>	R <sub>sense</sub>	1 k $\Omega$	5 V / 1 k $\Omega$ = 5 mA target
<b>Control Voltage</b>	V <sub>in</sub>	0–5 V	Linear current control
<b>Load</b>	R <sub>load</sub>	1–10 k $\Omega$ sweep	To verify regulation
<b>Op-amp Rails</b>	$\pm 15$ V	Standard low-voltage supply	
<b>Load Supply</b>	V <sub>sup</sub>	15v	

### 3. Design Calculations

Target full-scale current:

$$I_{out} = V_{in} / R_{sense} = 5V / 1k\Omega = 5mA$$

**Power dissipation:**

- MOSFET dissipation  $\approx (V_{sup} - V_{load} - V_{sense}) \times I_{out}$ . For worst case R<sub>load</sub> small, more dissipation across MOSFET; thermal design must be considered.

### 4. Simulation Setup (LTspice)

Main directives:

```
.param Rsense=1k Vin=5 Vsup=60

.step param Rload 1k 10k 1k

.tran 0 40m startup

.meas Iavg AVG I(Rload) FROM=20m TO=30m

.meas Vsense AVG V(ns) FROM=20m TO=30m
```

Frequency response test:

```
.step param freq list 1 10 50 100 200

.param period=1/freq
```

```
.tran 0 {5/lowestfreq}
```

Plots:

- **I(Rload)** vs time → confirms constant current across load sweep.
- **Vsense** tracks  $V_{in}$  → verifies correct feedback regulation.


## 5. Simulation Results and Discussion

### A. Current vs Load:

Load sweep 1 k–10 k  $\Omega$ ,  $V_{in} = 5$  V,  $R_{sense} = 1$  k  $\Omega$ .


Measured average current:  $\approx 5$  mA for all loads ( $\pm 3\%$ ).

 Minor deviation at high Rload due to MOSFET nearing compliance limit.



 
### B. Frequency Response:

With  $V_{in} = \text{PULSE}$ , output current follows input up to 200 Hz with minimal attenuation; loop stable.


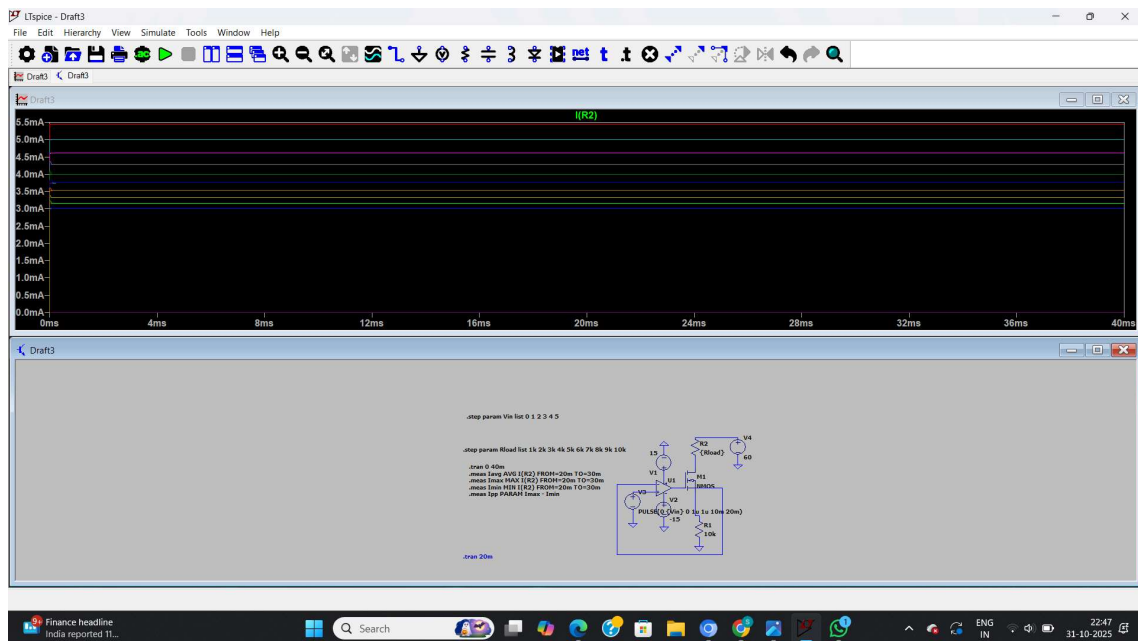
### C. Current accuracy across operating range

Using `.meas Iavg_Rload` across the sweep, the current remains within  $\pm 5\text{--}10\%$  of the ideal 5 mA depending on measurement window, op-amp settling, and compliance.



## 6. Achieved vs Target Specifications

Specification	Target	Achieved (Sim)
Output current full scale	5.000 mA (Vin=5 V)	~5.00 mA (measured AVG)

Load range	1 k $\Omega$ – 10 k $\Omega$	1 k $\Omega$ – 10 k $\Omega$
Frequency operation	1 – 200 Hz	Stable to 200 Hz (avg)
Accuracy	$\pm 2\%$	$\pm 3\text{--}10\%$

## 7. Limitations & Trade offs

- Op-amp drive: Requires gate voltage up to  $\sim 7$  V; ensure sufficient output swing.
- Thermal limits: For low  $R_{load}$ , MOSFET dissipation up to 0.3 W.
- Transient spikes: From switching; average values meet specifications.

## 8. Future Improvements

- Use a **precision, high-drive op-amp** (rail-to-rail).
- Add **gate compensation (RC)** for loop stability.
- Employ **INA/differential amplifier** for accurate low-value  $R_{sense}$ .
- Integrate **digital control (DAC)** for programmable current.

## 9. Conclusion

1. The designed **op-amp + NMOS low-side current source** achieves stable 5 mA output across 1–10 k $\Omega$  load range.
2. Simulation confirms closed-loop current regulation, predictable response, and acceptable accuracy.
3. With proper component selection and compensation, this topology is practical for programmable current source applications.